



# ARDUINO CAPACITANCE METER

A PROJECT BY

MEEMANSA PANDEY(2022102036) AND HIMANI SHARMA(2022102032)



# COMPONENTS REQUIRED

- ARDUINO UNO
- 16\*2 LCD DISPLAY
- 10K OHM POTENTIOMETER
- 10K OHM RESISTOR
- 220 OHM RESISTOR
- JUMPER WIRES
- CAPACITOR UNDER TEST

# DESCRIPTION

- A capacitance meter is a device that is used to measure capacitance of a capacitor.
- In this project, we will develop two circuits-
  - a) CIRCUIT1 - to measure capacitance in the range of  $1\mu\text{F}$  to  $4700\mu\text{F}$
  - b) CIRCUIT2 - to measure capacitance in the range of  $20\text{pF}$  to  $1000\text{nF}$
- BASIC PRINCIPLE - The Time Constant ( $\tau$ )



An unknown capacitor is charged through a known resistor using Arduino pins. The time taken for the voltage across capacitor to reach 63.2% of the supply voltage gives us the value of  $\tau$ .

$$C = \frac{\tau}{R}$$
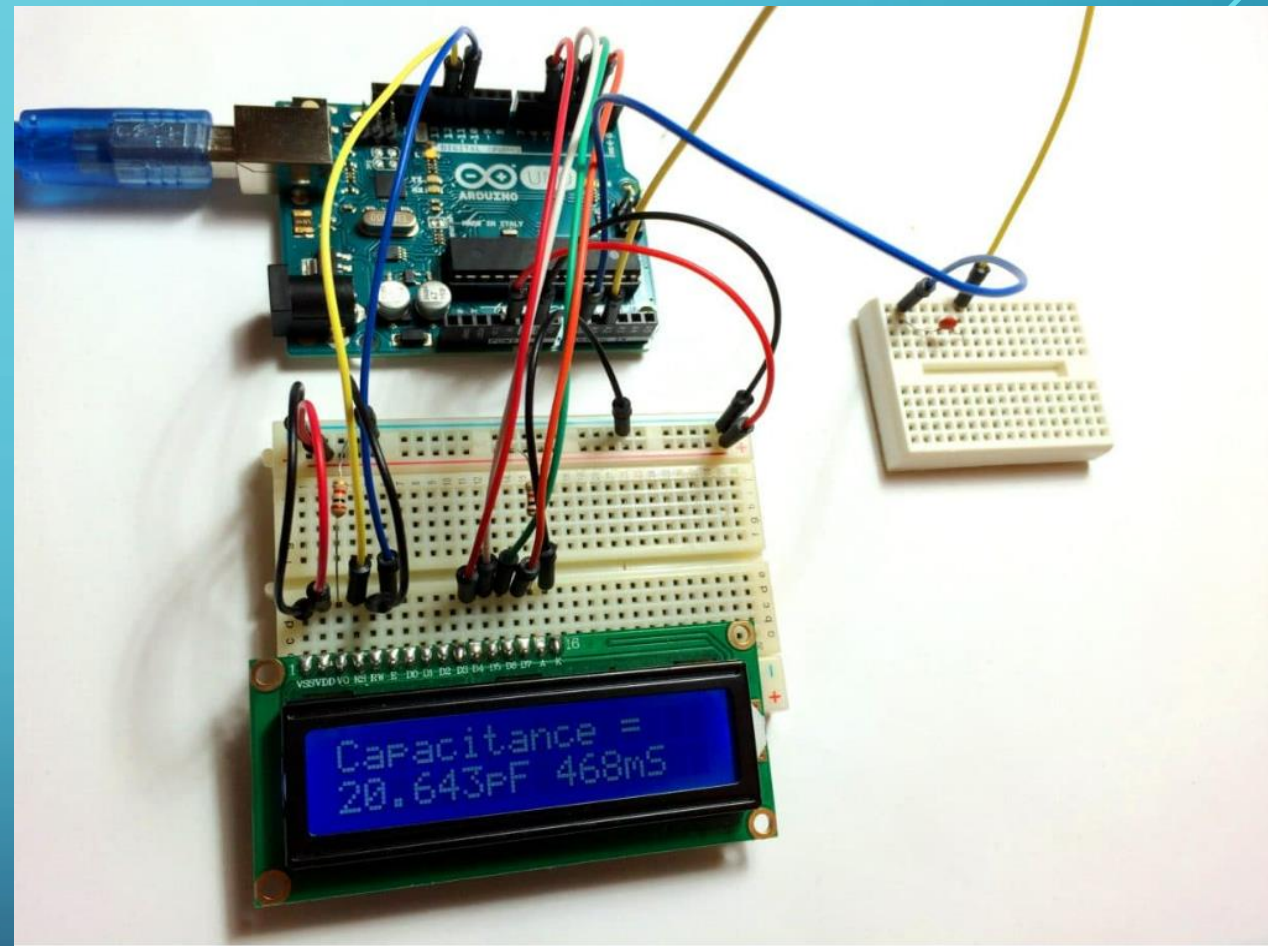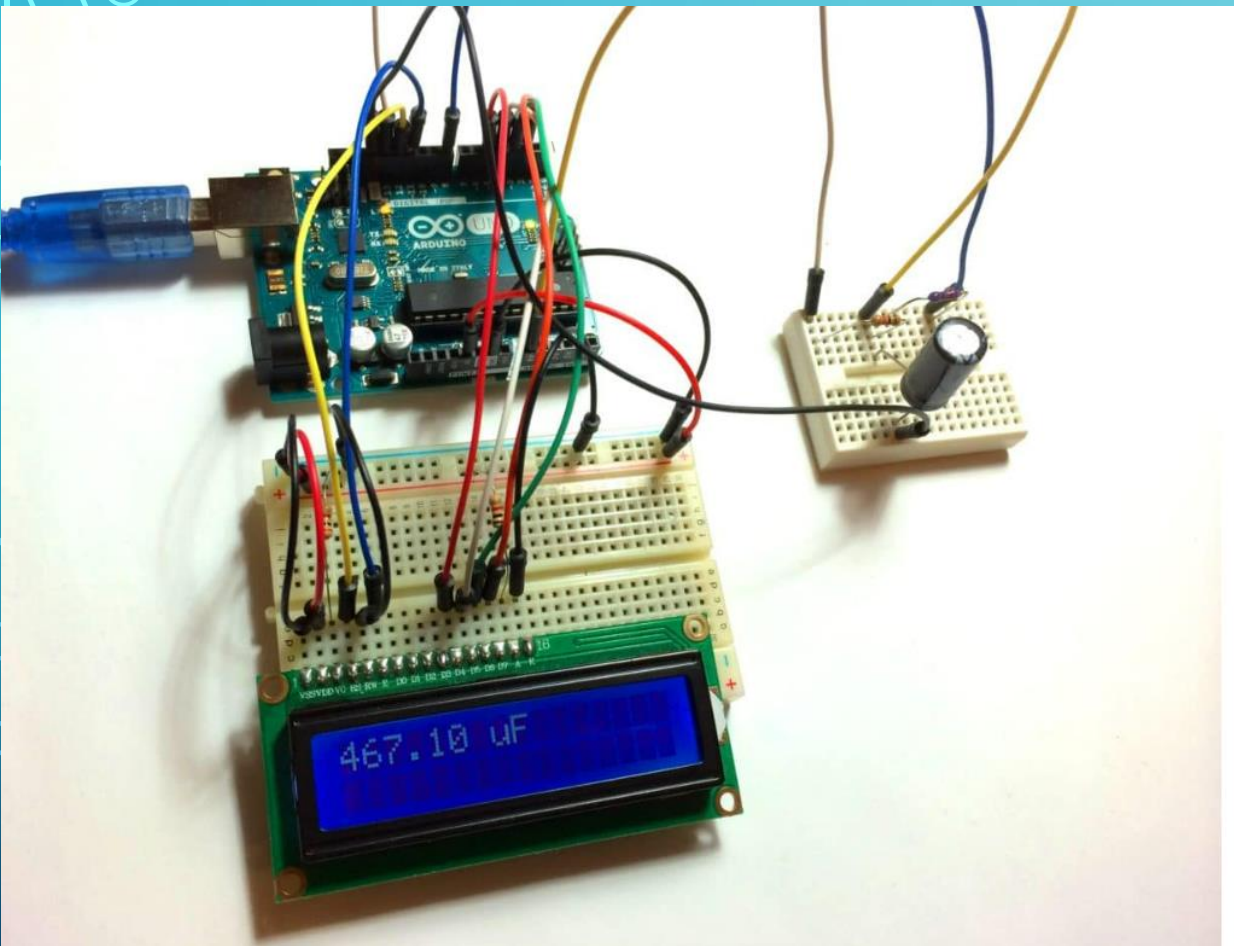
# NEED FOR TWO CIRCUITS



- All the I/O ports in ATmega328P Microcontroller have an internal pull – up resistor and an internal capacitor connected between the pin and ground.
- The value of internal capacitance ranges from 20-30pF.
- For large values of capacitance of the test capacitor, voltage drop across the internal capacitor is negligible and almost the entire supply voltage is obtained across the unknown capacitor.
- But for small values of capacitance of the test capacitor, the supply voltage gets divided among the test and the internal capacitor in direct ratios of their capacitances.

$$v_{C_t} = v_s * \left( \frac{C_t}{C_t + C_i} \right)$$





# CIRCUIT DIAGRAMS

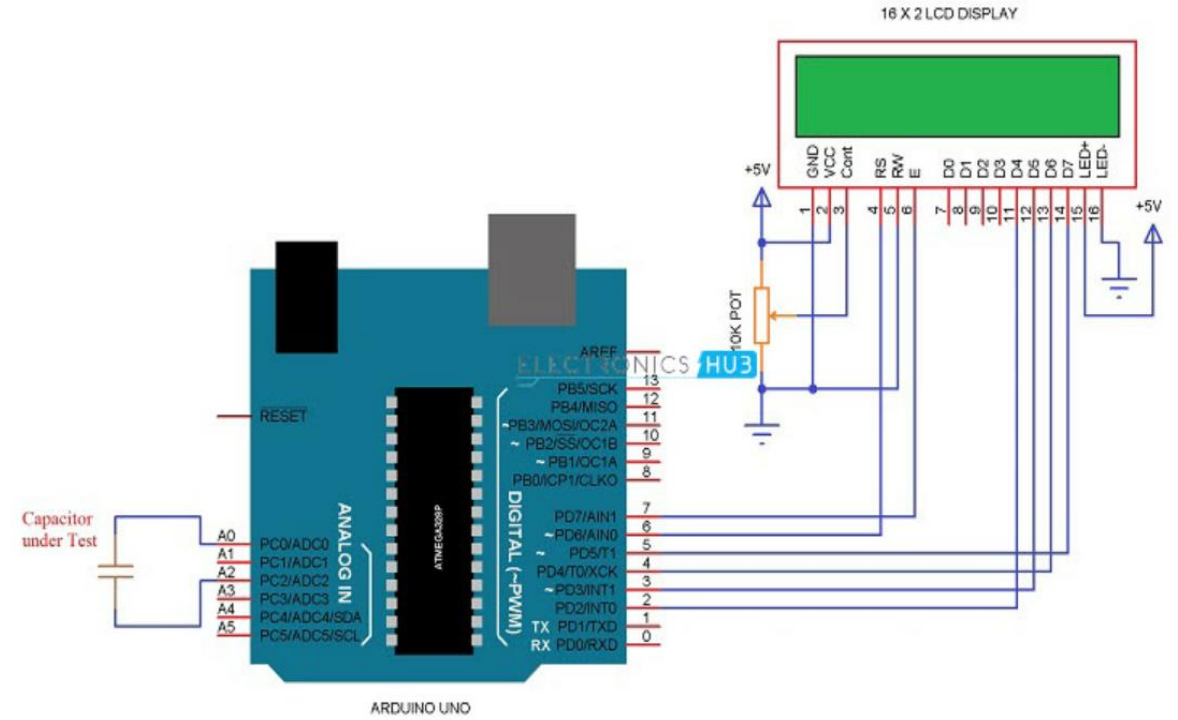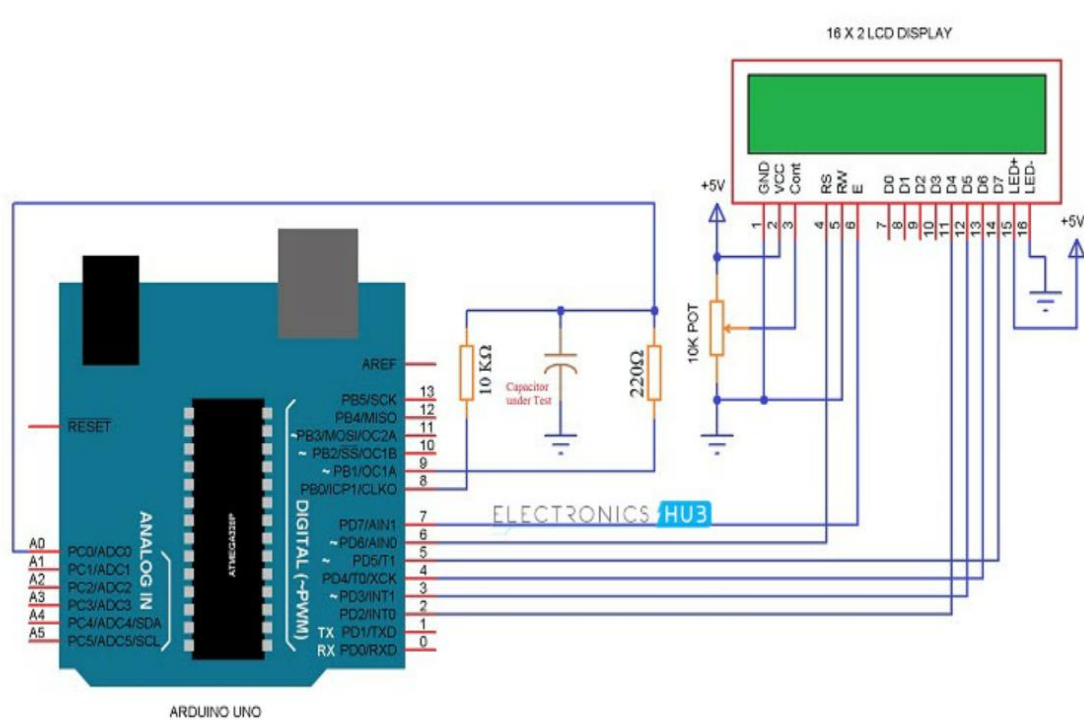



# TIMELINE

- COMPLETION OF CIRCUIT 1 - 30/01/2023
- COMPLETION OF CIRCUIT 2 - 03/02/2023
- COMPLETION OF PROJECT - 05/02/2023
- FINAL TEST OF THE PROJECT – 06/02/2023